

Submitted By :
Snehal Gupta
2016201

Moore Circuit :

Clock divider :

```
//clk_div.v
`timescale 1ns / 1ps
module clk_div(
input wire mclk,
output wire clk190);
reg [18:0] q;
always @(posedge mclk)
begin
q <= q+1;
end
assign clk190 = q[18];
endmodule
```

Debouncer :

[illegible]

```

module debounce(
    input clk_in,
    input clr_in,
    output clr_out
);
    reg D1,D2,D3;
    always@(posedge clk_in)
    begin
        D1 <= clr_in;
        D2 <= D1;
        D3 <= D2;
    end
    assign clr_out = D1 && D2 && D3;
endmodule

```

Clock_pulse generator:

//clock_pulse.v

```

`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 26.09.2017 18:04:34
// Design Name:
// Module Name: clock_pulse
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////
module clock_pulse(
    input wire inp,
    input wire cclk,
    input wire clr,

```

```

output wire outp);
reg delay1;
reg delay2;
reg delay3;
always@(posedge cclk or posedge clr)
begin
if(clr == 1)
begin
delay1 <= 1'b0;
delay2 <= 1'b0;
delay3 <= 1'b0;
end
else
begin
delay1 <= inp;
delay2 <= delay1;
delay3 <= delay2;
end
end
assign outp = delay1 & delay2 & delay3;
endmodule

```

Moore circuit:

```

//moore.v
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 04.10.2017 16:54:21
// Design Name:
// Module Name: moore
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//

```

////////////////////////////////////////////////////////////////

```
module moore(
    input clk,
    input clr,
    input din,
    output reg dout,
    output reg [2:0] present_state
);
    reg[2:0] next_state;
    parameter S0=3'b000 , S1=3'b001 , S2=3'b010 , S3=3'b011 , S4=3'b100 , S5=3'b101 ;
    always@(posedge clk or posedge clr)
    begin
        if(clr == 1)
            present_state <= S0;
        else
            present_state <= next_state;
        end
        always@(*)
        begin
            case(present_state)
                S0 : if(din == 1)
                    next_state <= S1;
                    else
                        next_state <= S0;
                S1 : if(din == 0)
                    next_state <= S2;
                    else
                        next_state <= S1;
                S2 : if(din == 1)
                    next_state <= S3;
                    else
                        next_state <= S0;
                S3 : if(din == 0)
                    next_state <= S4;
                    else
                        next_state <= S1;
                S4 : if(din == 1)
                    next_state <= S5;
                    else
                        next_state <= S0;
                S5 : if(din == 0)
```

```

        next_state <= S0;
    else
        next_state <= S1;
    default next_state <= S0;
endcase
end
always@(*)
begin
    if(present_state == S5)
        dout <= 1;
    else
        dout <= 0;
    end
end

endmodule

```

Top module:

//top.v

`timescale 1ns / 1ps

////////////////////////////////////////////////////////////////

// Company:

// Engineer:

//

// Create Date: 04.10.2017 17:15:19

// Design Name:

// Module Name: top

// Project Name:

// Target Devices:

// Tool Versions:

// Description:

//

// Dependencies:

//

// Revision:

// Revision 0.01 - File Created

// Additional Comments:

//

////////////////////////////////////////////////////////////////

module top(

input clk,

input clr,

```

input [1:0] btn,
output [1:0] led,
output [2:0] present_state
);
wire inp;
assign inp= btn[0] || btn[1];
clk_div CD1(.mclk(clk),.clk190(clk_190));
debounce D1(.clk_in(clk_190),.clr_in(clr),.clr_out(clr_de));
clock_pulse CP(.inp(inp),.cclk(clk_190),.clr(clr_de),.outp(out_pulse));
moore M1(.clk(out_pulse),.clr(clr_de),.din(btn[1]),.dout(led[0]),.present_state(present_state));
assign led[1] = out_pulse;
endmodule

```

Mealy circuit :

//Clock_divider,clock_pulse and debouncer remains the same.

//top.v

```

`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 04.10.2017 17:15:19
// Design Name:
// Module Name: top
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////

```

```

module top(
    input clk,
    input clr,

```

```

input [1:0] btn,
output [1:0] led,
output [2:0] present_state
);
wire inp;
assign inp= btn[0] || btn[1];
clk_div CD1(.mclk(clk),.clk190(clk_190));
debounce D1(.clk_in(clk_190),.clr_in(clr),.clr_out(clr_de));
clock_pulse CP(.inp(inp),.cclk(clk_190),.clr(clr_de),.outp(out_pulse));
mealy M1(.clk(out_pulse),.clr(clr_de),.din(btn[1]),.dout(led[0]),.present_state(present_state));
assign led[1] = out_pulse;
endmodule

```

//mealy.v

```

`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 04.10.2017 16:54:21
// Design Name:
// Module Name: moore
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////

```

```

module mealy(
    input clk,
    input clr,
    input din,
    output reg dout,
    output [2:0] present_state
);
    reg[2:0] next_state;
    parameter S0=3'b000 , S1=3'b001 , S2=3'b010 , S3=3'b011 , S4=3'b100;
    always@(posedge clk or posedge clr)
    begin
        if(clr == 1)

```

```

begin
next_state <= S0;
dout <= 0;
end
else
case(present_state)
S0 : if(din == 1)
    begin
        next_state <= S1;
        dout <= 0;
    end
    else
    begin
        next_state <= S0;
        dout <= 0;
    end
S1 : if(din == 0)
    begin
        next_state <= S2;
        dout <= 0;
    end
    else
    begin
        next_state <= S1;
        dout <= 0;
    end
S2 : if(din == 1)
    begin
        next_state <= S3;
        dout <= 0;
    end
    else
    begin
        next_state <= S0;
        dout <= 0;
    end
S3 : if(din == 0)
    begin
        next_state <= S4;
        dout <= 0;
    end
    else
    begin
        next_state <= S1;
        dout <= 0;
    end
S4 : if(din == 1)
    begin
        next_state <= S0;
        dout <= 1;
    end

```



```

        end
    else
    begin
        next_state <= S0;
        dout <= 0;
    end
    default:
    begin
        next_state <= S0;
        dout <= 0;
    end
    endcase
    end
    assign present_state=next_state;

endmodule

```

//const.xdc

```

set_property PACKAGE_PIN W5 [get_ports {clk}]
set_property IOSTANDARD LVCMOS33 [get_ports {clk}]
set_property PACKAGE_PIN T17 [get_ports {clr}]
set_property IOSTANDARD LVCMOS33 [get_ports {clr}]
set_property PACKAGE_PIN W19 [get_ports {btn[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {btn[1]}]
set_property PACKAGE_PIN U18 [get_ports {btn[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {btn[0]}]
set_property PACKAGE_PIN L1 [get_ports {led[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {led[1]}]
set_property PACKAGE_PIN P1 [get_ports {led[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {led[0]}]
set_property PACKAGE_PIN N3 [get_ports {present_state[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {present_state[2]}]
set_property PACKAGE_PIN P3 [get_ports {present_state[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {present_state[1]}]
set_property PACKAGE_PIN U3 [get_ports {present_state[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {present_state[0]}]

```

Conclusion :

Mealy circuit :

Utilization - Post-Implementation				⤴
Resource	Utilization	Available	Utilization %	
LUT	11	20800	0.05	
FF	29	41600	0.07	
IO	9	106	8.49	
BUFG	1	32	3.12	

Moore circuit :

Utilization - Post-Implementation				⤴
Resource	Utilization	Available	Utilization %	
LUT	11	20800	0.05	
FF	28	41600	0.07	
IO	9	106	8.49	
BUFG	1	32	3.12	

Mealy consumes one flip-flop more than moore circuit .